







Lecture 5

- RC/RL First-Order Circuits

Beginning of **Temporal** Behavior Analysis
of Circuits



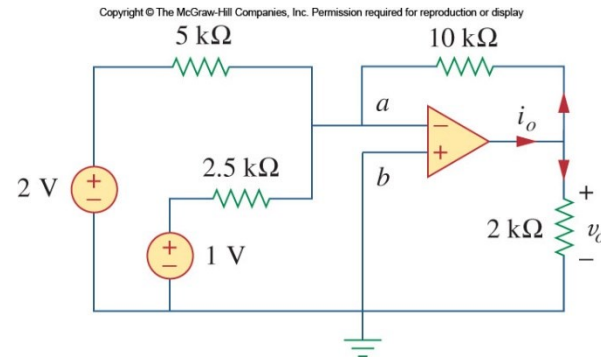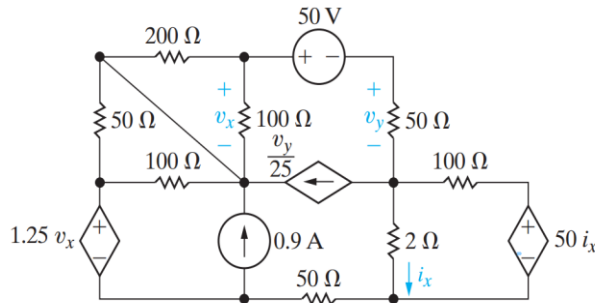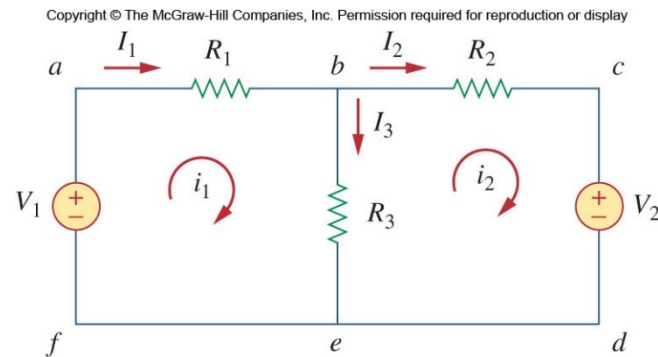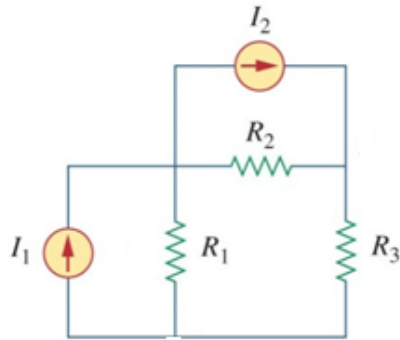- Till now we discussed static analysis of a circuit
 - Responses at a given time depend only on inputs at that time.
 - Circuit responds to input changes infinitely fast.






Outline

- Capacitors and inductors
- Natural response of RC/RL circuits
- Step response of RC/RL circuits
- Others



Capacitors


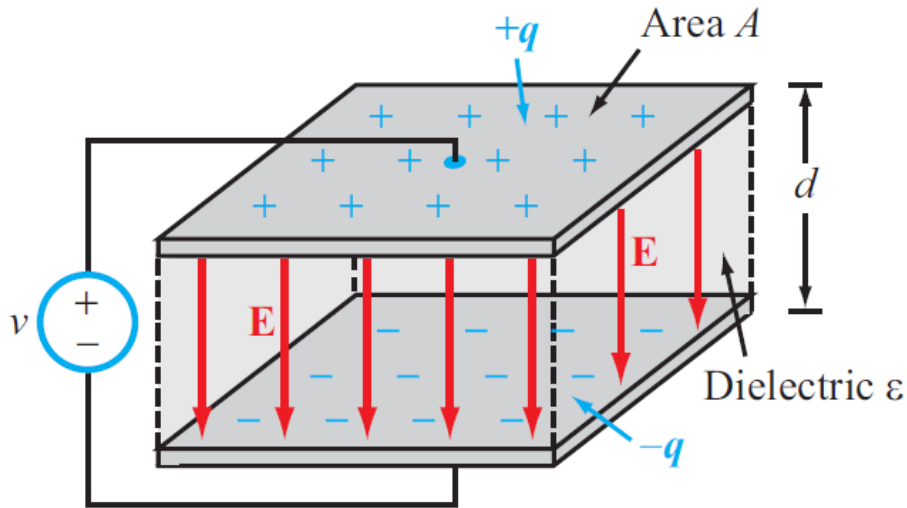
Storage element that stores energy in electric field



Parallel plate capacitor




V-I Relationship of Capacitors

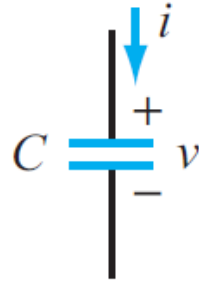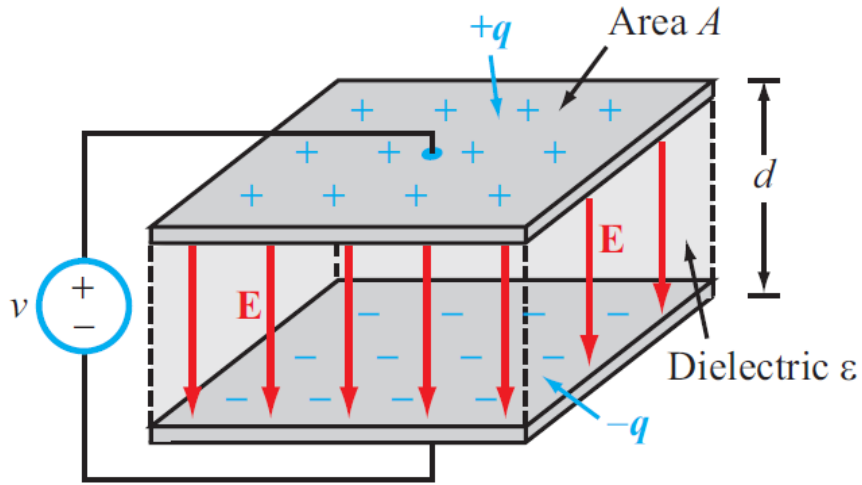




Stored Energy

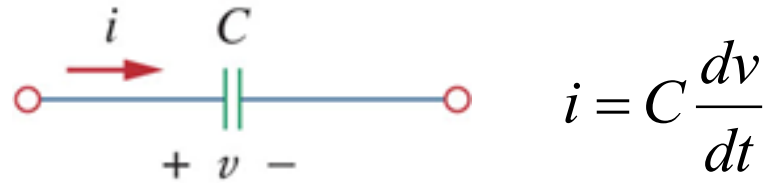


- The instantaneous power delivered to the capacitor is
- The energy stored in a capacitor is:






Example-1

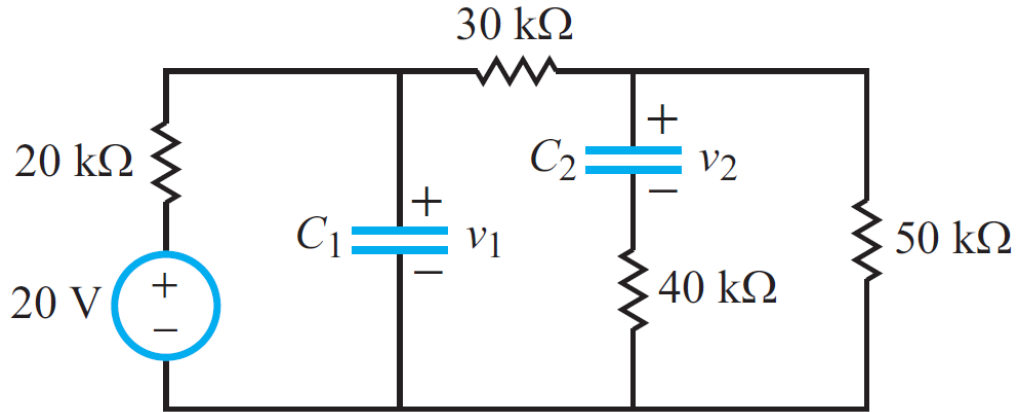


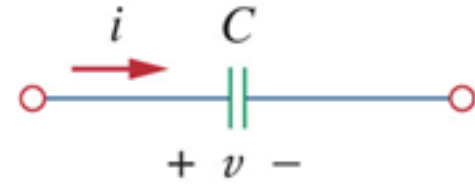


Example-2 Capacitor Response

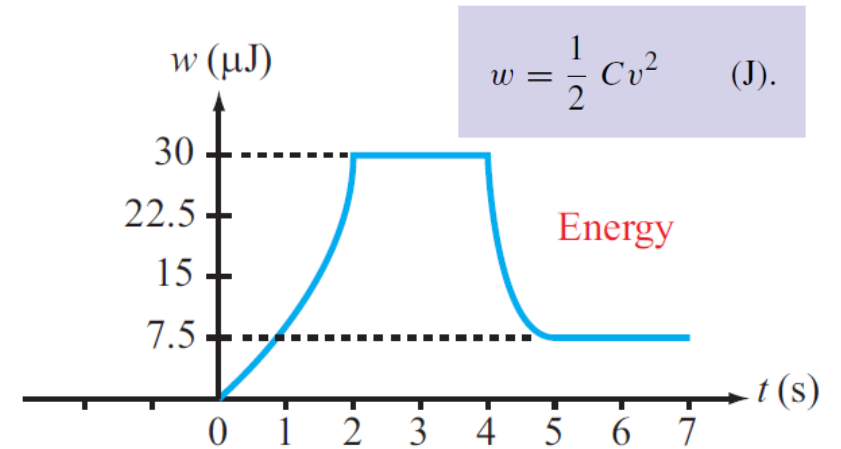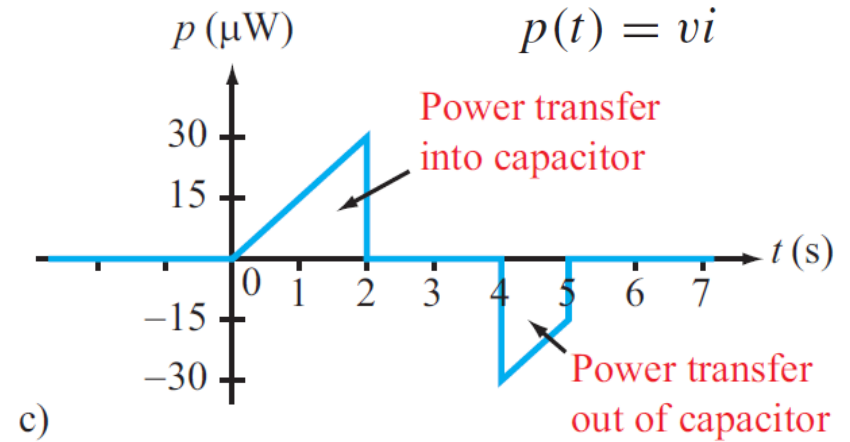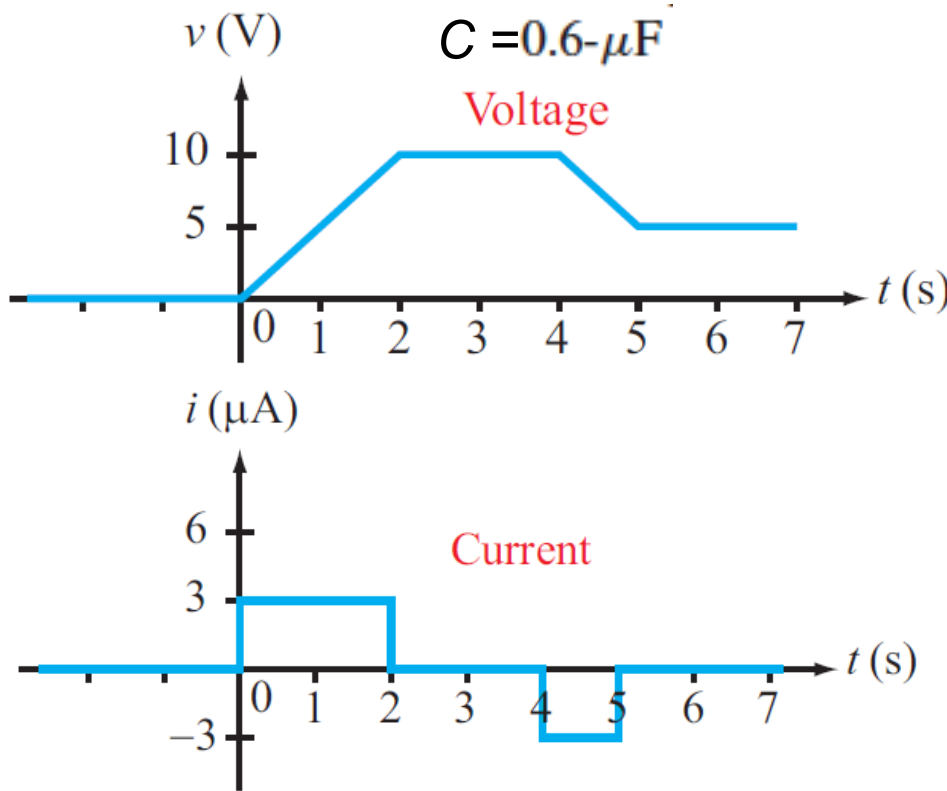





Important Property of Capacitors

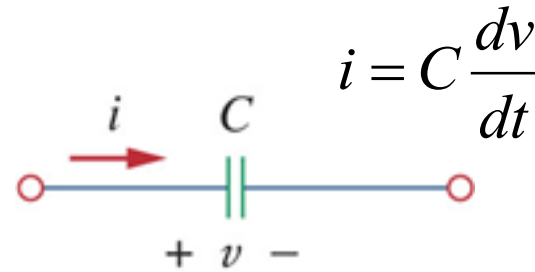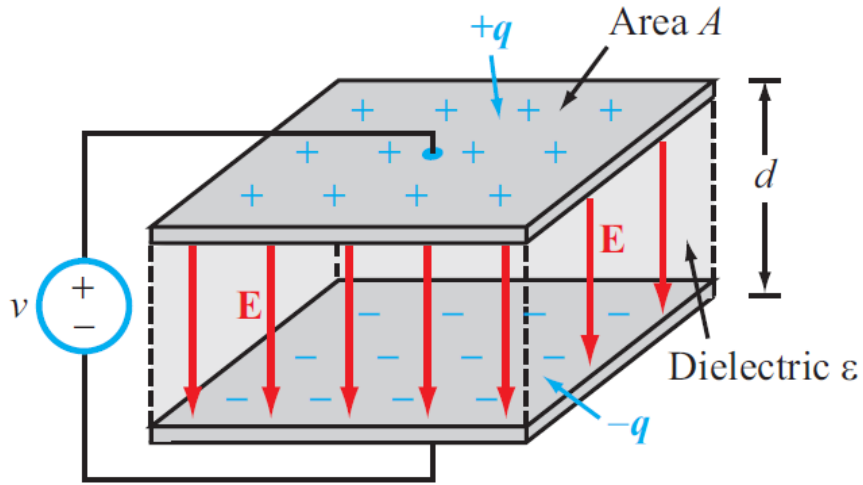

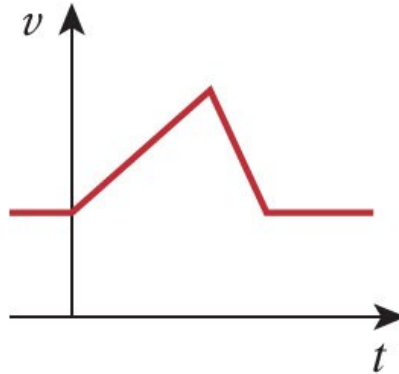Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



(a)


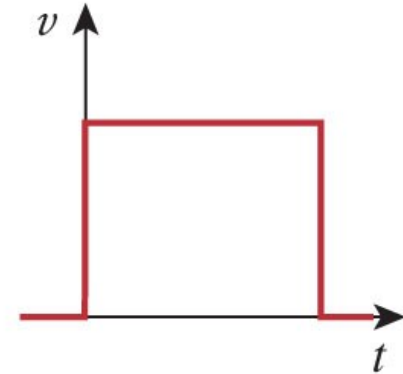


(b)





Capacitors in Series

Combining In-Series Capacitors

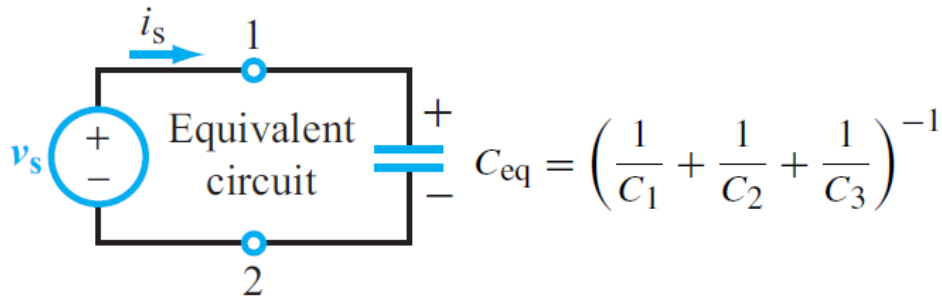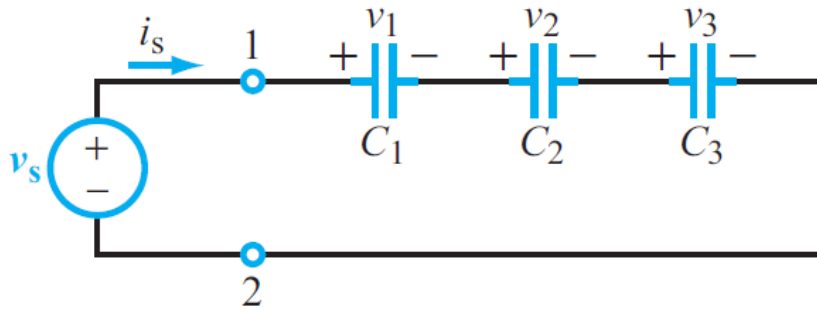




Capacitors in Parallel

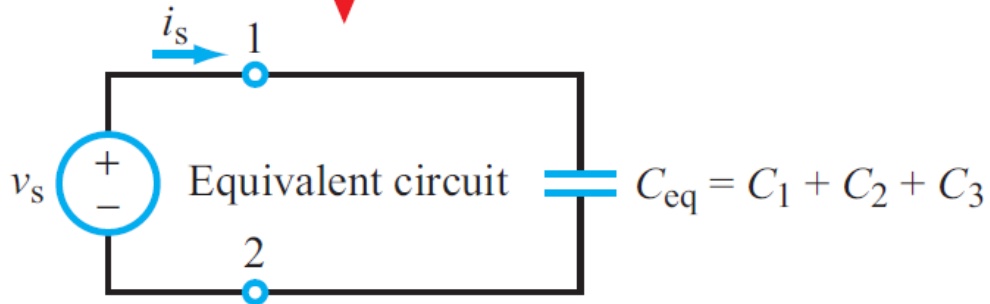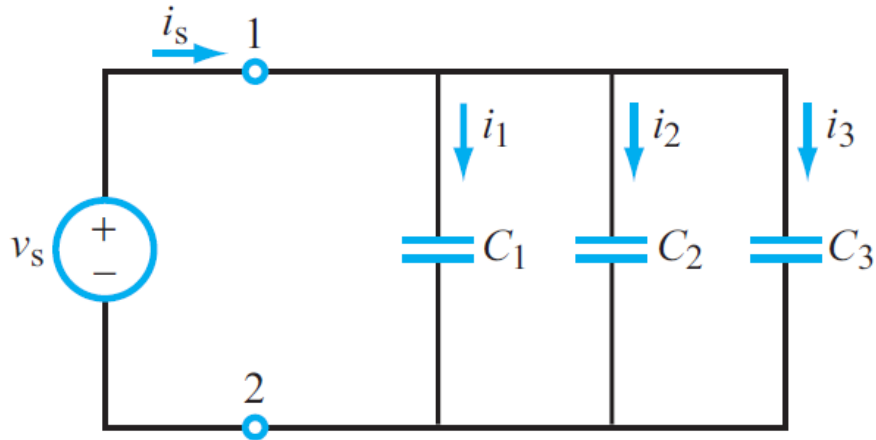


Inductors

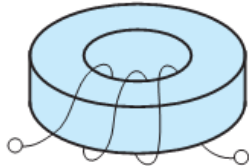
- A storage element that stores energy in magnetic field.
 - They have applications in power supplies, transformers, radios, TVs, radars, and electric motors.
- Any conductor has inductance, but the effect is typically enhanced by coiling the wire up.



(a) Toroidal inductor

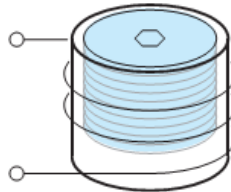


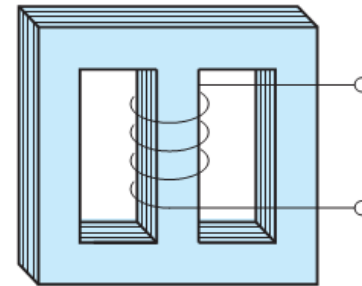
(b) Coil with an iron-oxide slug that can be screwed in or out to adjust the inductance



(c) Inductor with a laminated iron core



V-I Relationship of Inductors

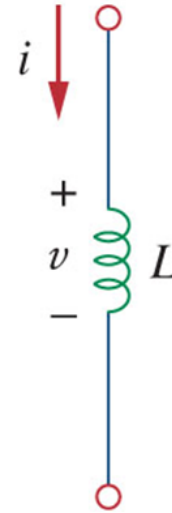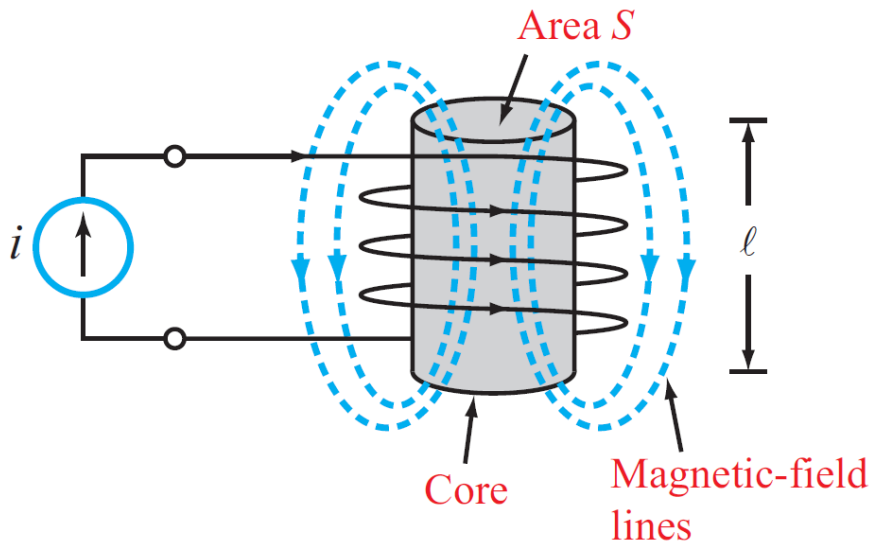


$$v = L \frac{di}{dt}$$




Energy Stored in an Inductor

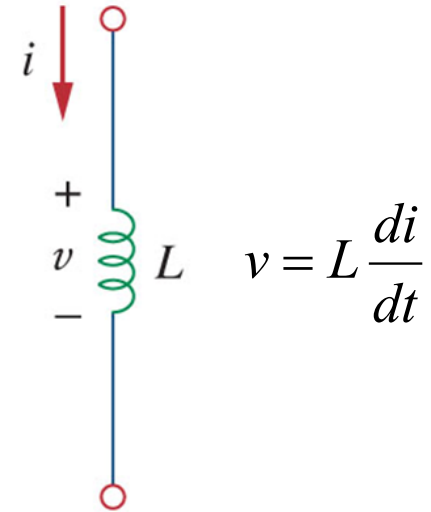- The power delivered to the inductor is:
- The energy stored is:






Inductor Response

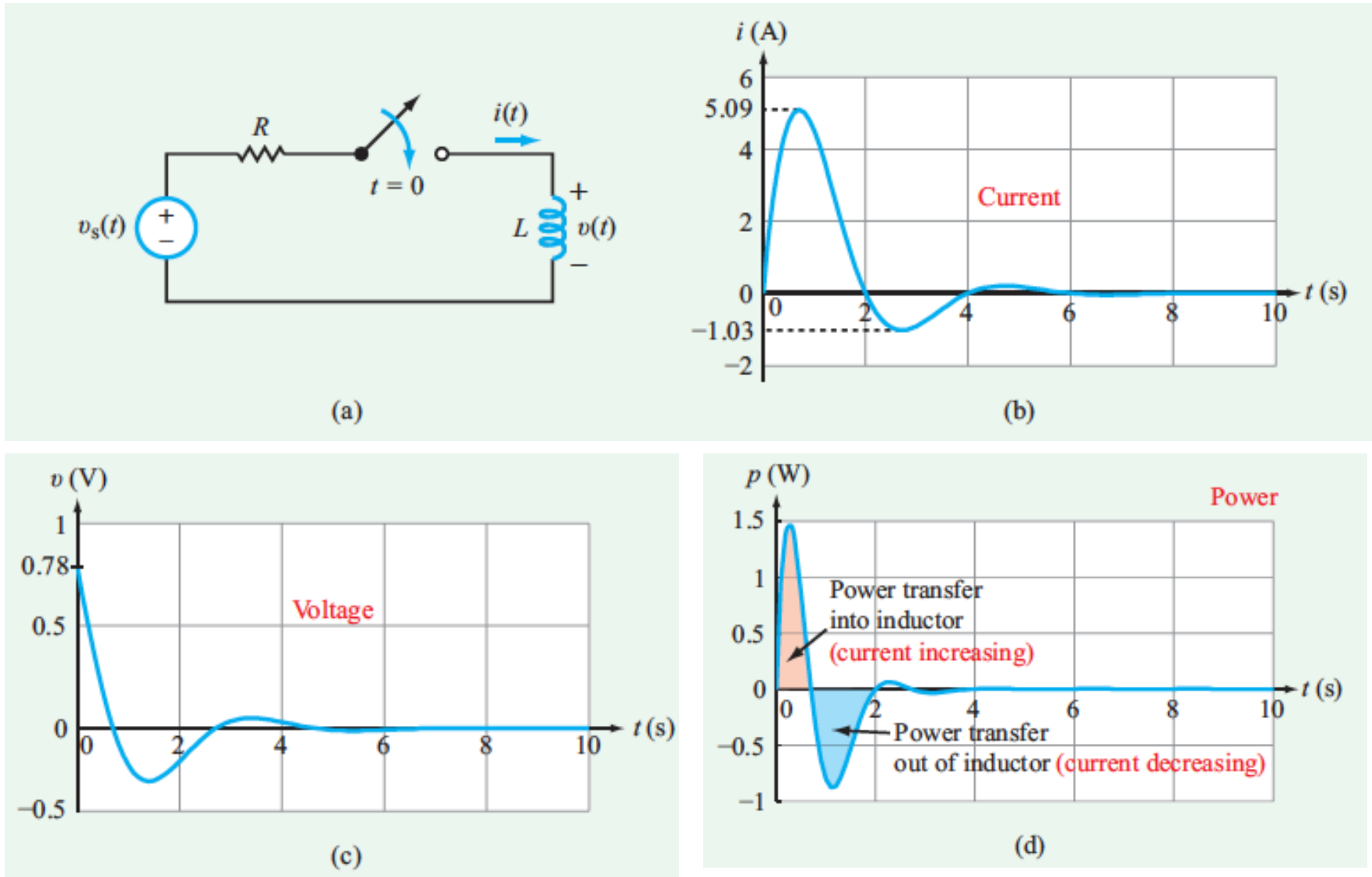





Important Property of Inductors

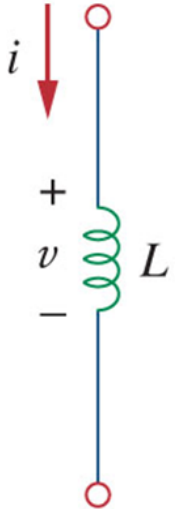



$$v = L \frac{di}{dt}$$

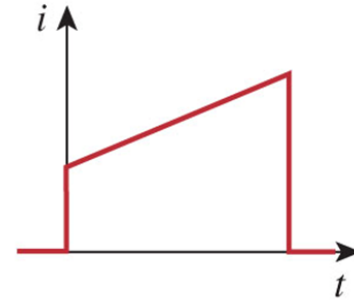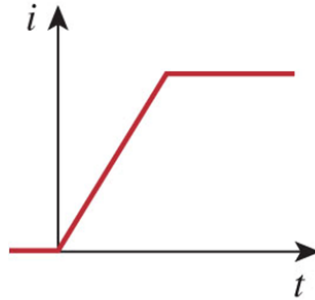Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display







Inductors in Series

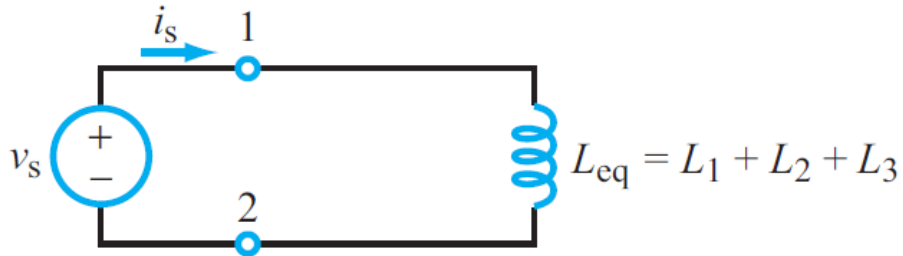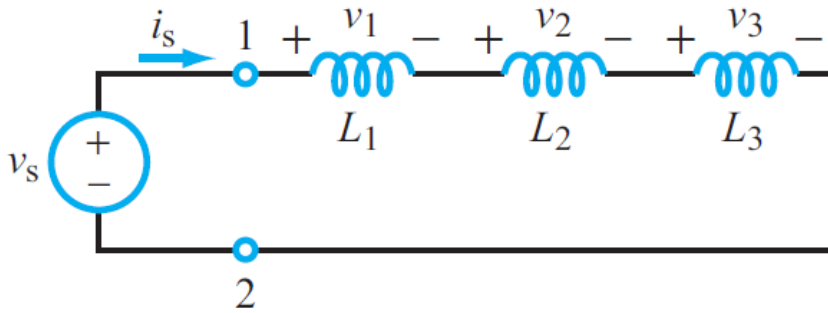



Inductors in Parallel



Combining In-Parallel Inductors

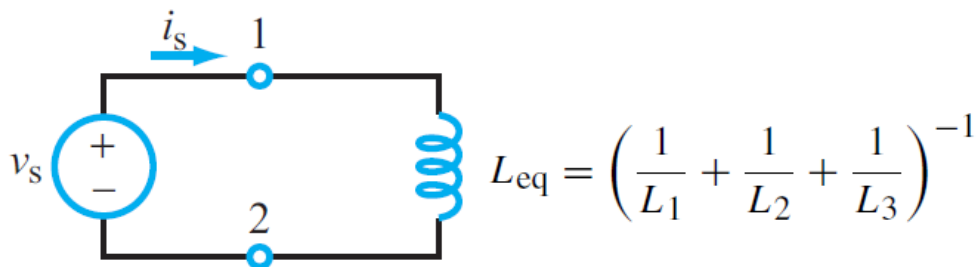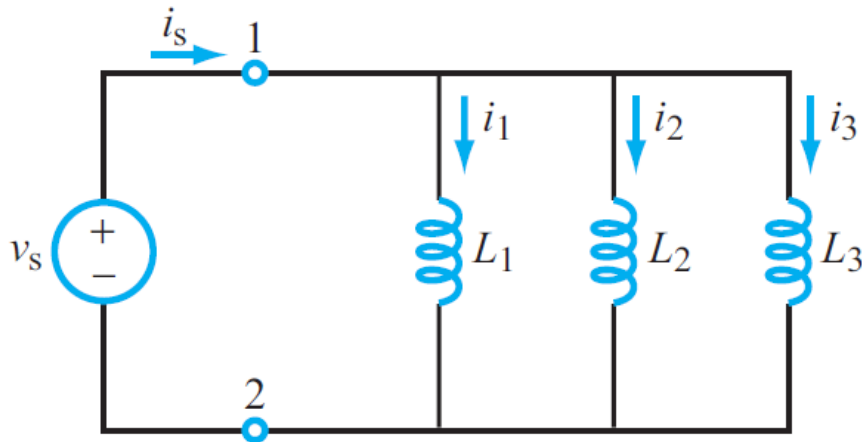

$$L_{eq} = \left(\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \right)^{-1}$$



Example

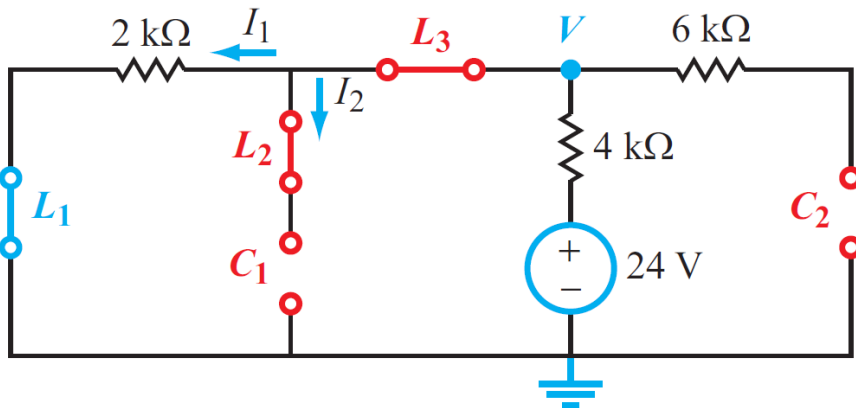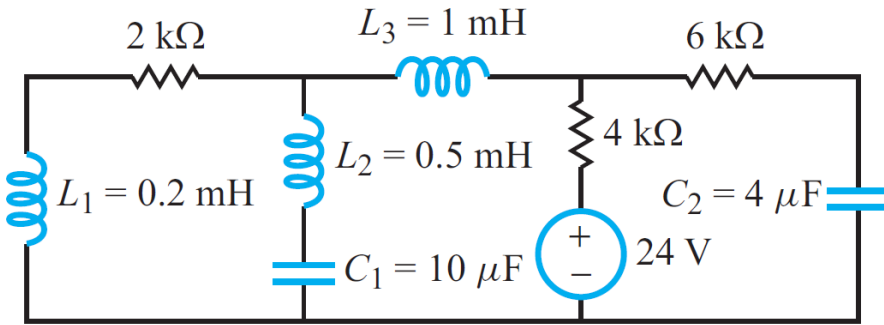



Summary of Resistors, Capacitors and Inductors

Table 5-4: Basic properties of R , L , and C .

Property	R	L	C
$i-v$ relation	$i = \frac{v}{R}$	$i = \frac{1}{L} \int_{t_0}^t v dt' + i(t_0)$	$i = C \frac{dv}{dt}$
$v-i$ relation	$v = iR$	$v = L \frac{di}{dt}$	$v = \frac{1}{C} \int_{t_0}^t i dt' + v(t_0)$
p (power transfer in)	$p = i^2 R$	$p = Li \frac{di}{dt}$	$p = Cv \frac{dv}{dt}$
w (stored energy)	0	$w = \frac{1}{2} Li^2$	$w = \frac{1}{2} Cv^2$
Series combination	$R_{eq} = R_1 + R_2$	$L_{eq} = L_1 + L_2$	$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$
Parallel combination	$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$	$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$	$C_{eq} = C_1 + C_2$
dc behavior	no change	short circuit	open circuit
Can v change instantaneously?	yes	yes	no
Can i change instantaneously?	yes	no	yes





Outline

- Capacitors and inductors
- Natural response of RC/RL circuits
- Step response of RC/RL circuits
- Others

RC and RL Circuits

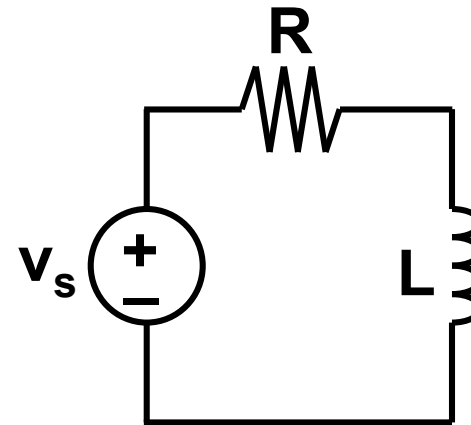
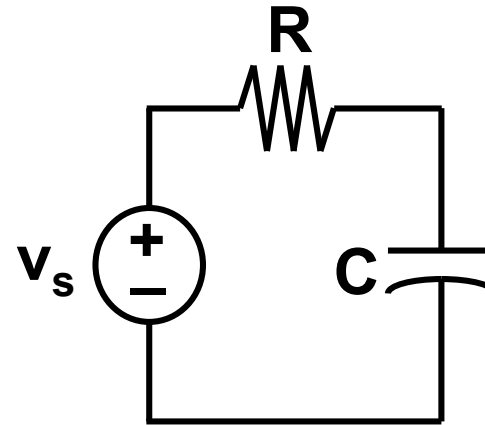
- A circuit that contains only source(s), resistor(s) and a capacitor is called an **RC circuit**.
- A circuit that contains only source(s), resistor(s) and an inductor is called an **RL circuit**.



Natural Response


Behavior (*i.e.*, current and voltage) when stored energy in the inductor or capacitor is released to the resistive part of the network (containing no independent sources).

Natural Response of a Charged Capacitor

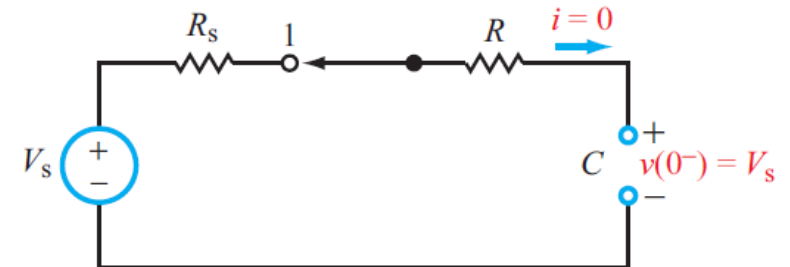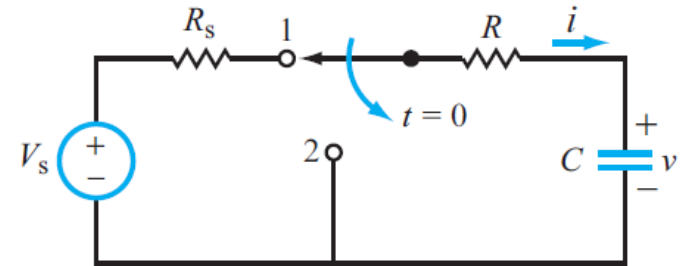


(a) $t = 0^-$ is the instant just before the switch is moved from terminal 1 to terminal 2;

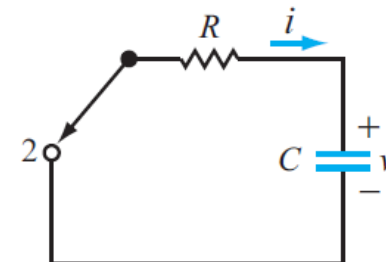(b) $t = 0$ is the instant just after it was moved, $t = 0$ is synonymous with $t = 0^+$.








Natural Response of a Charged Capacitor

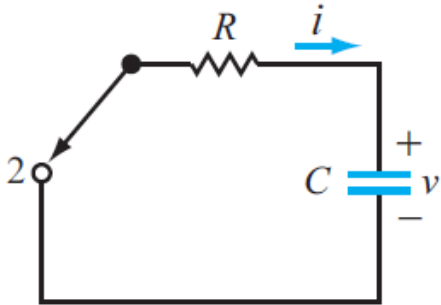





Natural Response of RC Circuit

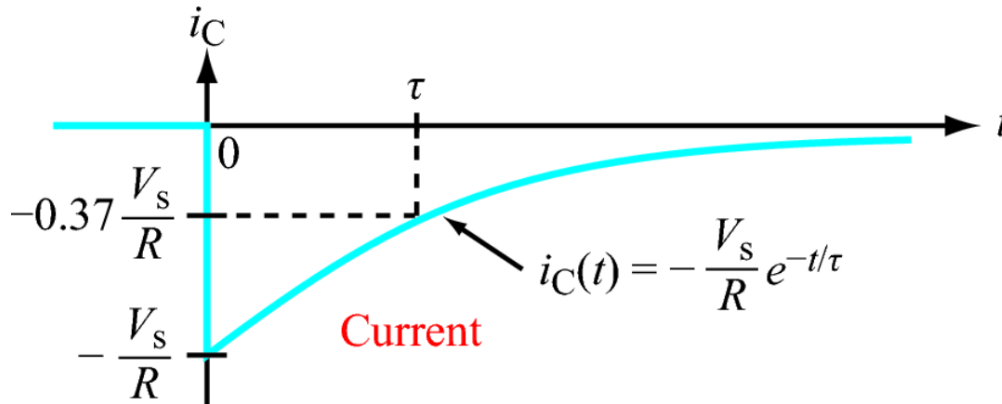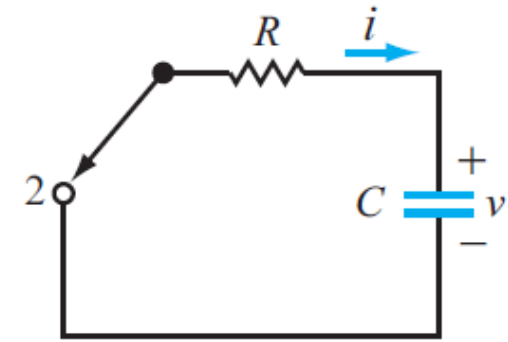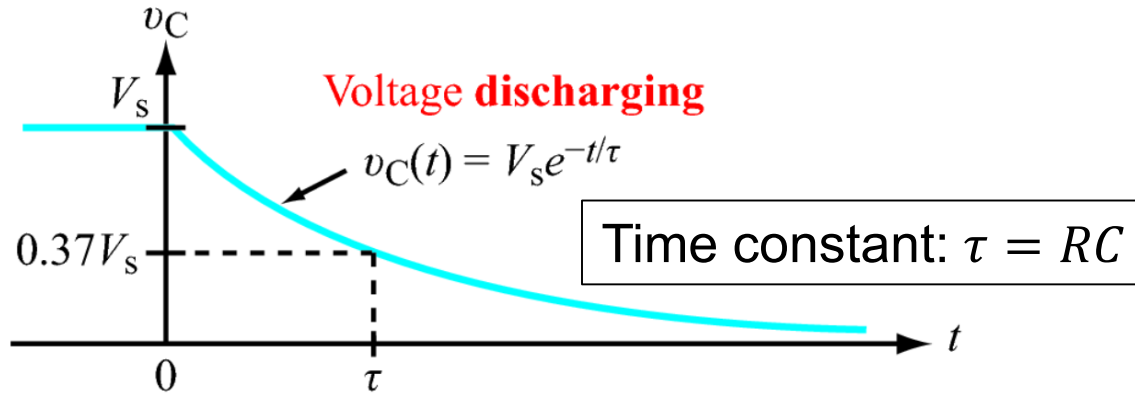

Time Constant $\tau (= RC)$




- A circuit with a small time constant has a fast response and vice versa.

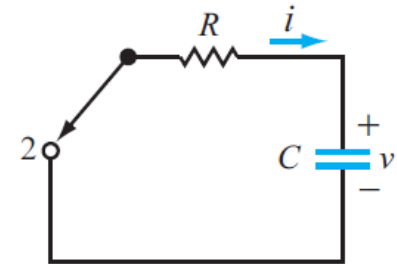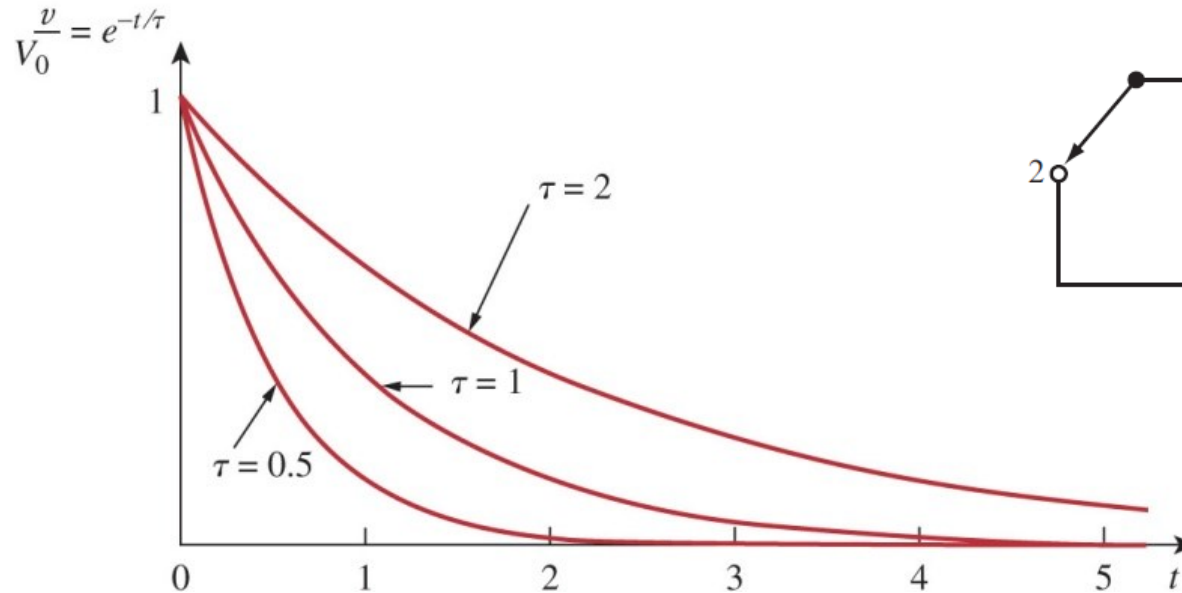Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display






Natural Response of the RL Circuit

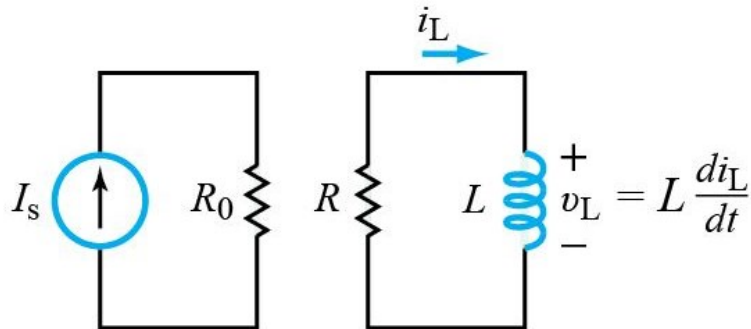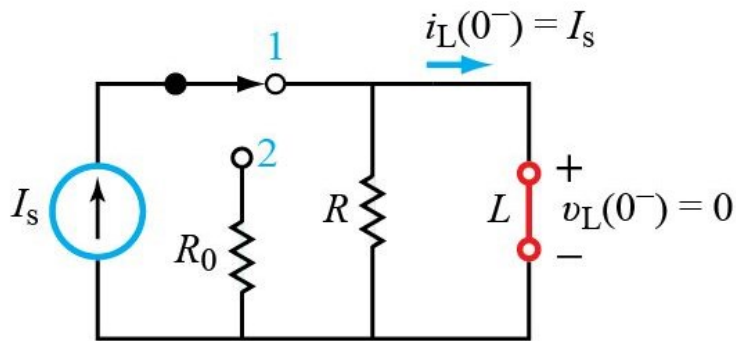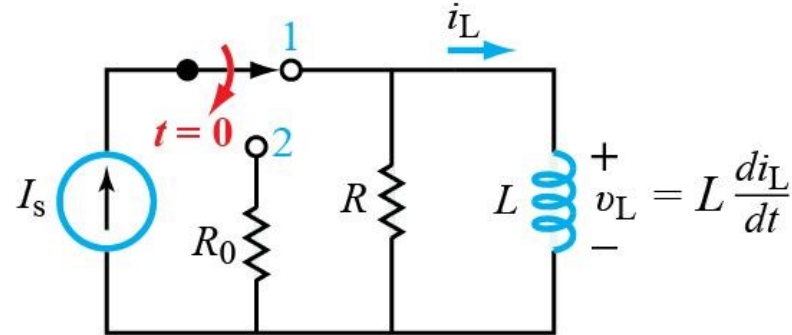




Natural Response of the RL Circuit

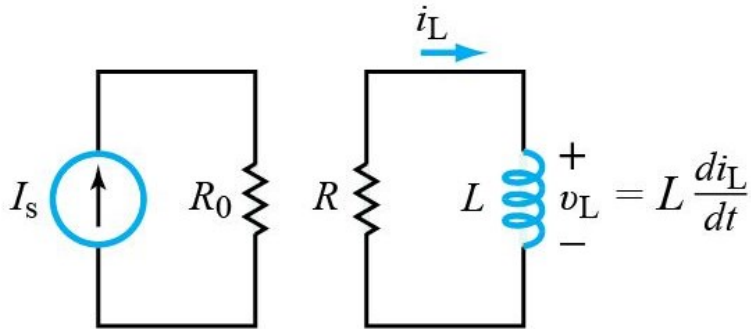




Natural Response of the RL Circuit

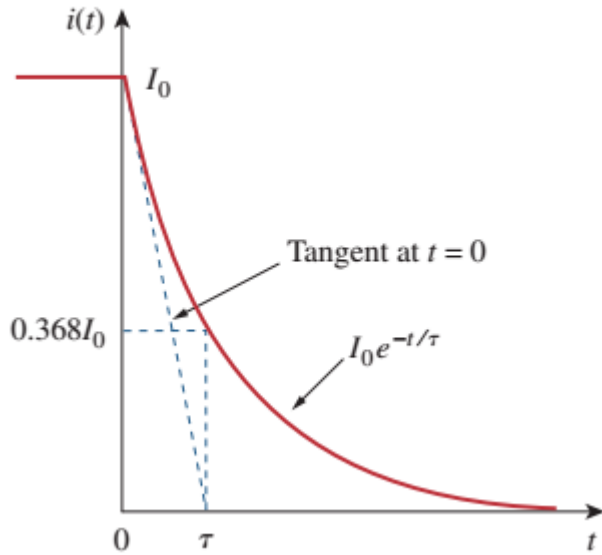



Natural Response Summary

RC Circuit

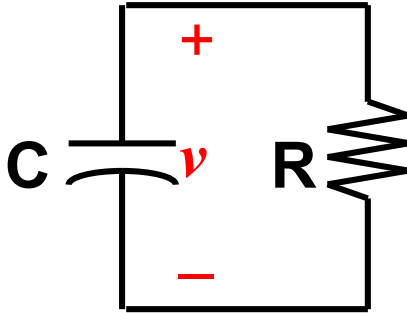


- **Capacitor voltage** cannot change instantaneously

$$v(0^-) = v(0^+)$$

$$v(t) = v(0)e^{-t/\tau}$$

- time constant $\tau = RC$

RL Circuit

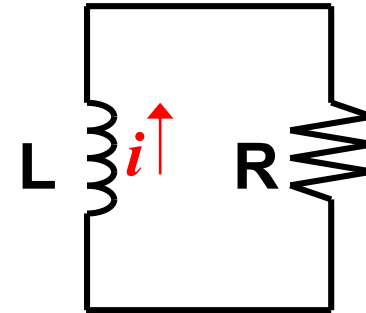

- **Inductor current** cannot change instantaneously

$$i(0^-) = i(0^+)$$

$$i(t) = i(0)e^{-t/\tau}$$


- time constant $\tau = \frac{L}{R}$



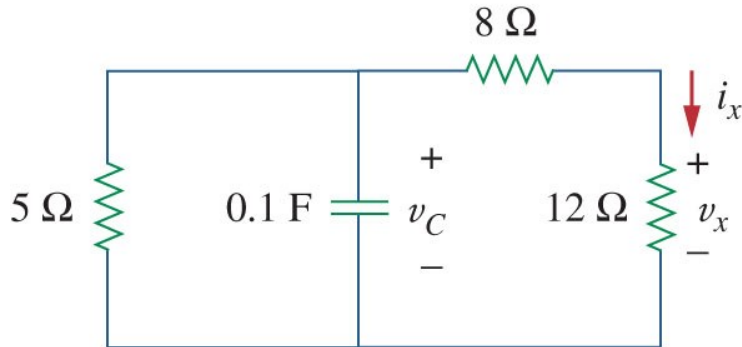Example

- In the circuit below, let $v_C(t = 0) = 15\text{V}$. Find v_C , v_x , and i_x for $t > 0$.


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display






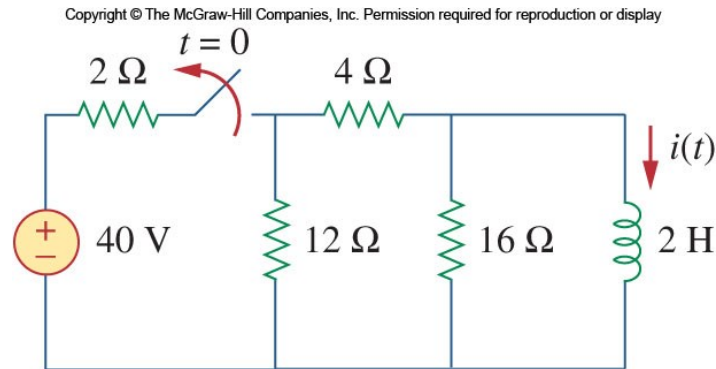Example


- The switch in the circuit below has been closed for a long time. At $t = 0$, the switch is opened. Calculate $i(t)$ for $t > 0$.



When $t < 0$

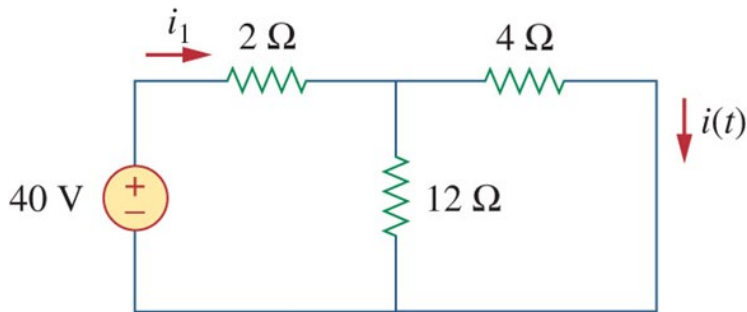

When $t > 0$

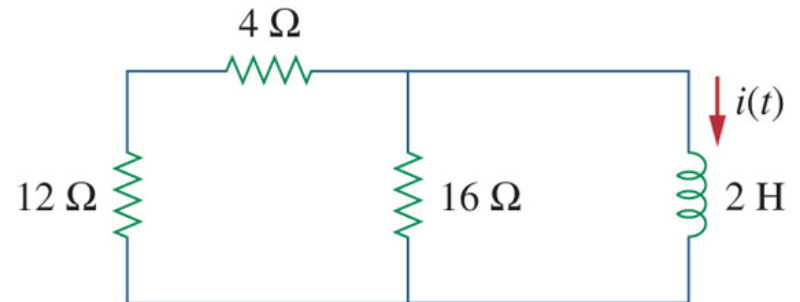




Outline

- Capacitors and inductors
- Natural response of RC/RL circuits
- Step response of RC/RL circuits
- Others

Step Response of RC Circuit

- When a **DC source** is suddenly applied to a RC circuit, the circuit response is known as the step response.

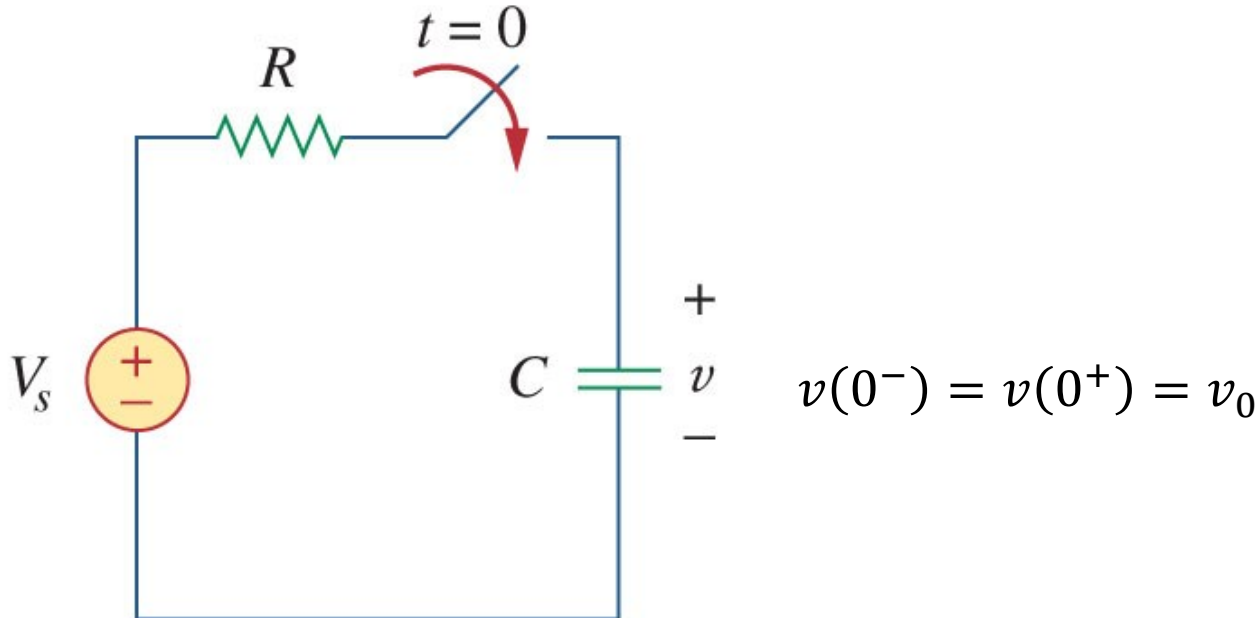Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display






The unit step function $u(t)$


- A step function is one that maintains a constant value before a certain time and then changes to another constant afterwards.

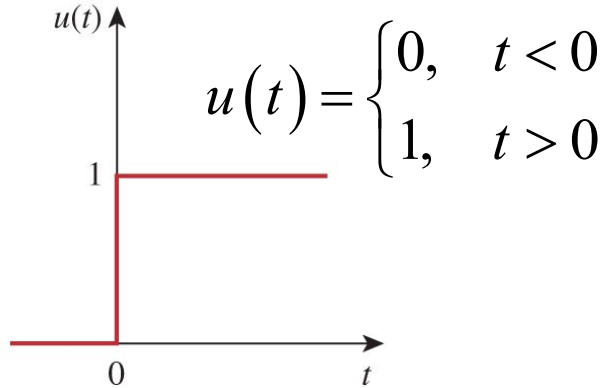Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




switching time may be shifted to $t = t_0$ by
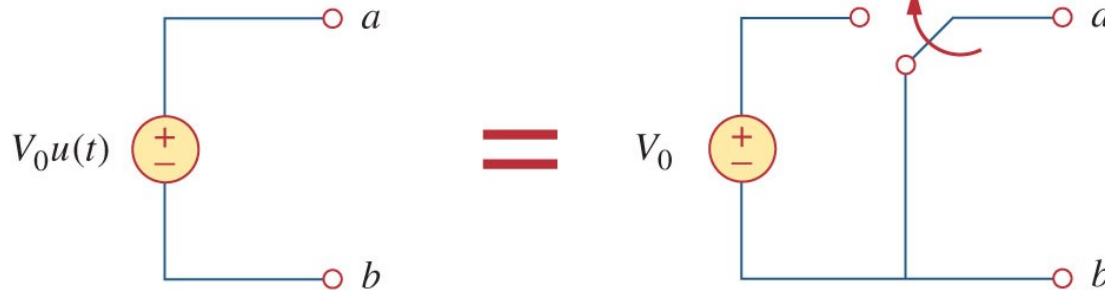
$$u(t - t_0) = \begin{cases} 0, & t < t_0 \\ 1, & t > t_0 \end{cases}$$




Equivalent Circuit of Unit Step

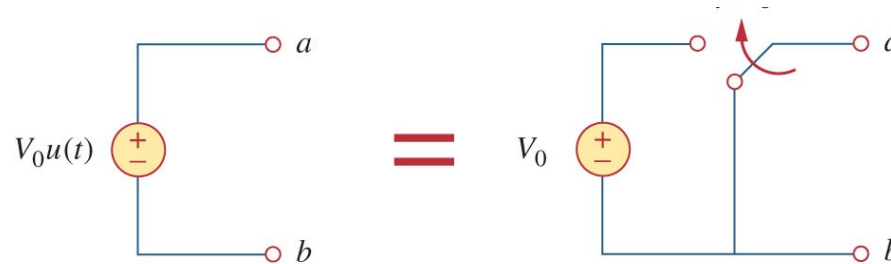- The unit step function has an equivalent circuit to represent when it is used **to switch on** a source.




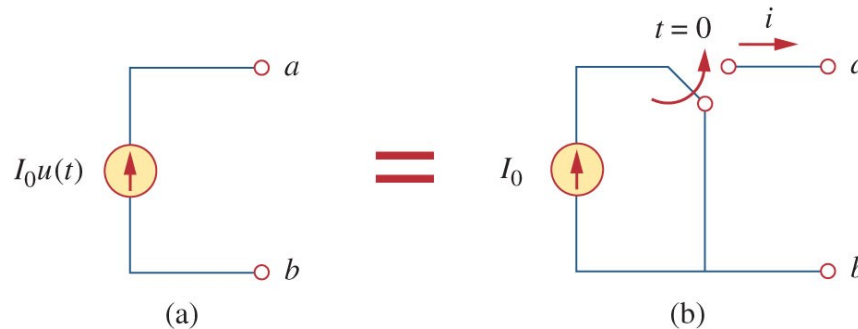Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





Step Response of the RC Circuit

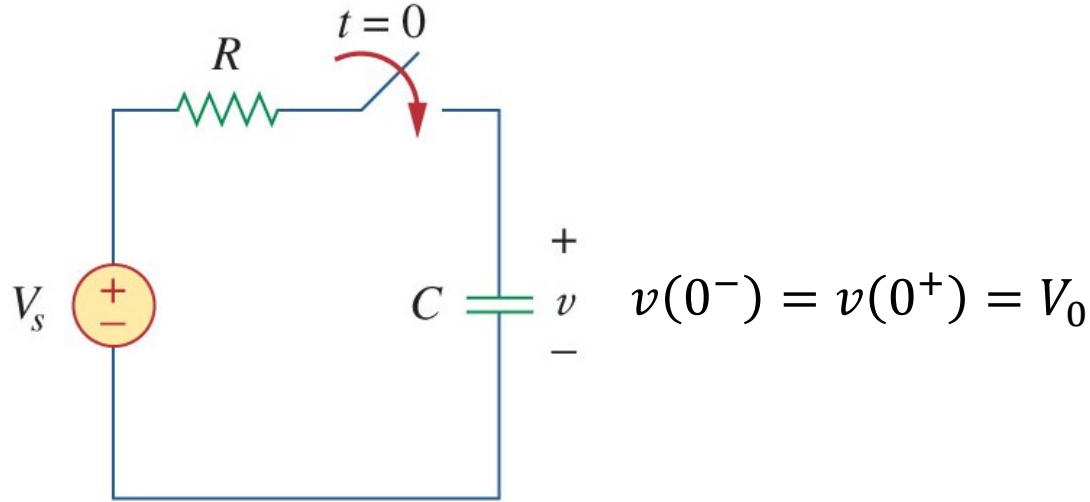






Step Response of the RC Circuit

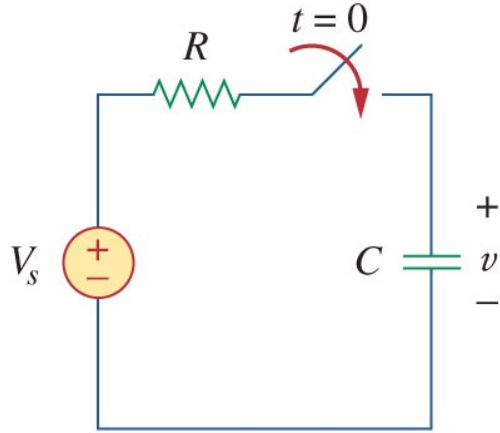
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



$$v(0^-) = v(0^+) = V_0$$

$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau} & t > 0 \end{cases}$$

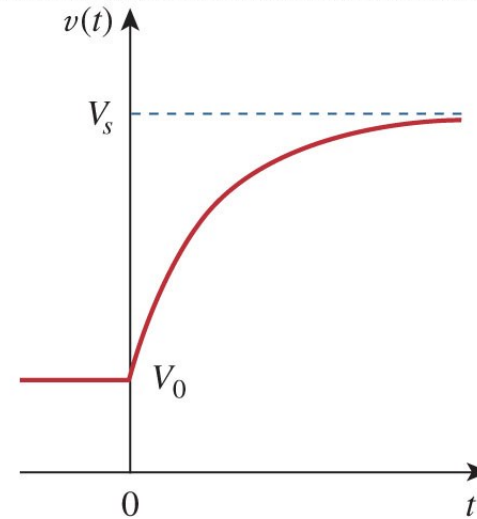Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




- This is known as the complete response, or total response.




Complete response

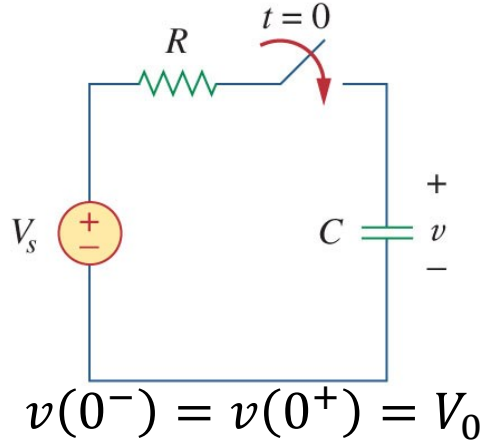Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



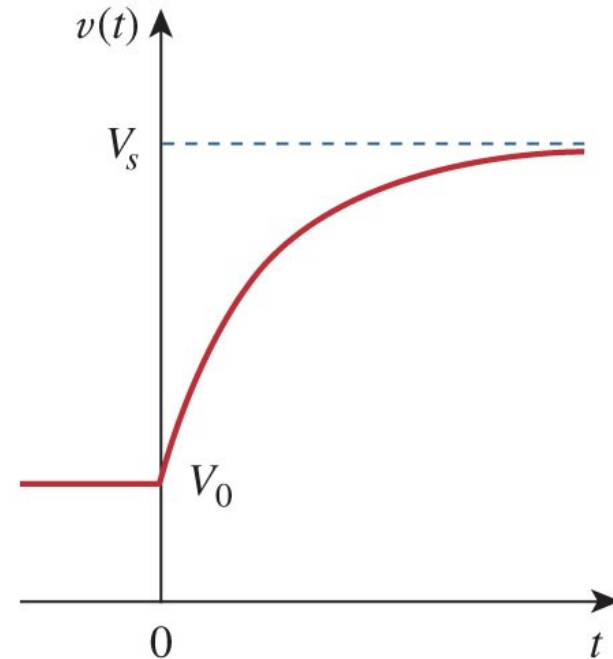Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



- The complete response


$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau} & t > 0 \end{cases}$$

can be written as:

$$v = v_n + v_f$$

Another Perspective
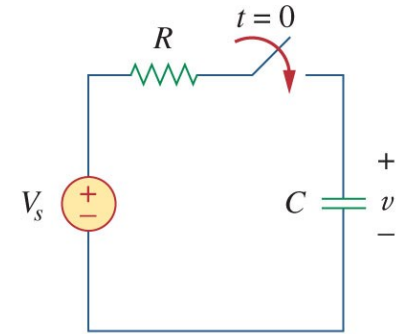
$$v(t) = \begin{cases} V_0, & t < 0 \\ V_s + (V_0 - V_s)e^{-t/\tau} & t > 0 \end{cases}$$




- Another way to look at the response is to break it up into the transient response and the steady state response:

$$v(t) = \underbrace{v(\infty)}_{\text{steady } v_{ss}} + \underbrace{[v(0) - v(\infty)]e^{-t/\tau}}_{\text{transient } v_t}$$



Step Response of the RL Circuit

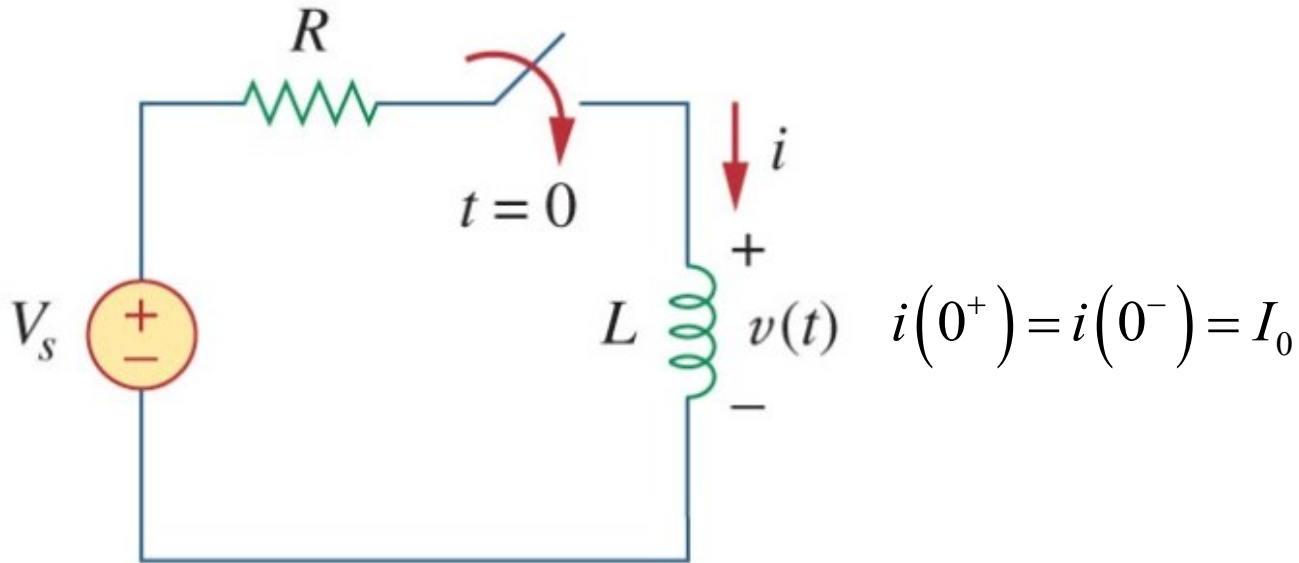Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display





$$i(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-t/\tau}$$

- Again one may break the response up into the transient response and the steady state response:

$$i(t) = \underbrace{i(\infty)}_{\text{steady } i_{ss}} + \underbrace{[i(0) - i(\infty)]e^{-t/\tau}}_{\text{transient } i_t}$$





General Procedure of Finding RC/RL Response with D.C. sources

1. Identify the variable of interest

- For RL circuits, it is usually the inductor current $i_L(t)$.
- For RC circuits, it is usually the capacitor voltage $v_c(t)$.

2. Determine the initial value of the variable at T_0

- Recall that $i_L(t)$ and $v_c(t)$ are continuous variables:

$$i_L(T_0^+) = i_L(T_0^-) \quad \text{and} \quad v_c(T_0^+) = v_c(T_0^-)$$

3. Determine the final value of the variable (as $t \rightarrow \infty$)

If needed, recall that an inductor behaves like a short circuit & that a capacitor behaves like an open circuit in steady state (e.g., $t \rightarrow \infty$).

4. Calculate the time constant for the circuit


- $\tau = CR$ for an RC circuit where R is the Thévenin equivalent resistance “seen” by the capacitor.
- $\tau = L/R$ for an RL circuit, where R is the Thévenin equivalent resistance “seen” by the inductor.





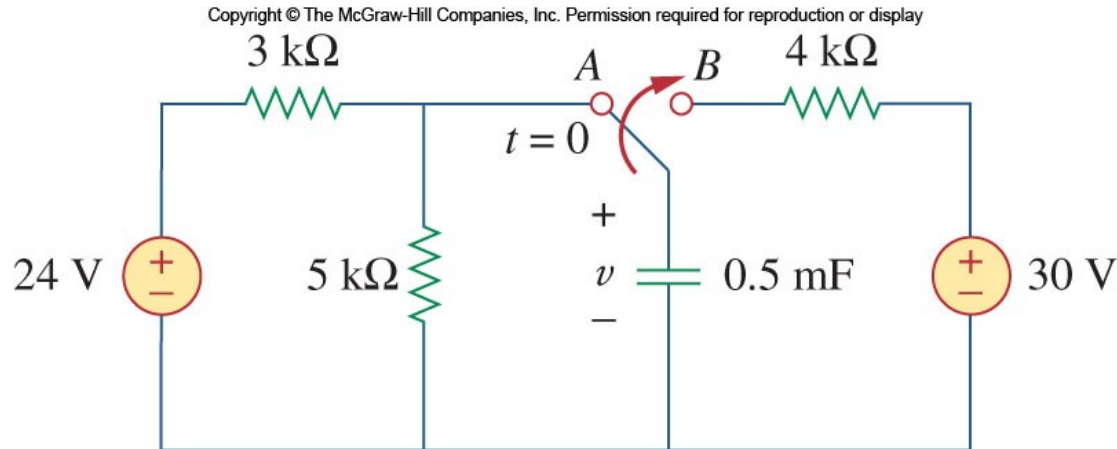Example

- The switch has been in position A for a long time. At $t = 0$, the switch moves to B. Find $v(t)$.






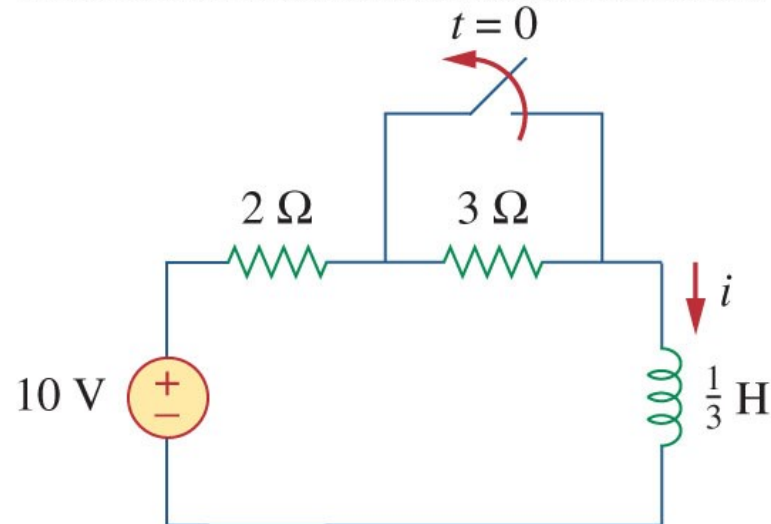Example


- Find $i(t)$ in the circuit for $t > 0$. Assume that the switch has been closed for a long time.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Sequential switch

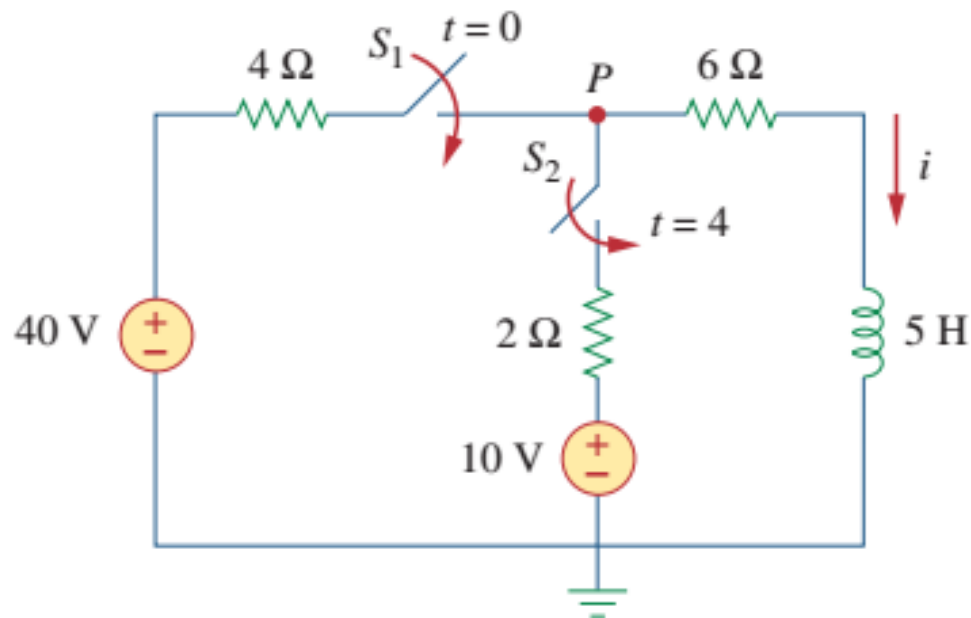At $t = 0$, switch 1 in Fig. 7.53 is closed, and switch 2 is closed 4 s later. Find $i(t)$ for $t > 0$. Calculate i for $t = 2$ s and $t = 5$ s.




We need to consider the three time intervals $t \leq 0$, $0 \leq t \leq 4$, and $t \geq 4$ separately. For $t < 0$, switches S_1 and S_2 are open so that $i = 0$. Since the inductor current cannot change instantly,

$$i(0^-) = i(0) = i(0^+) = 0$$



First order op-amp circuit

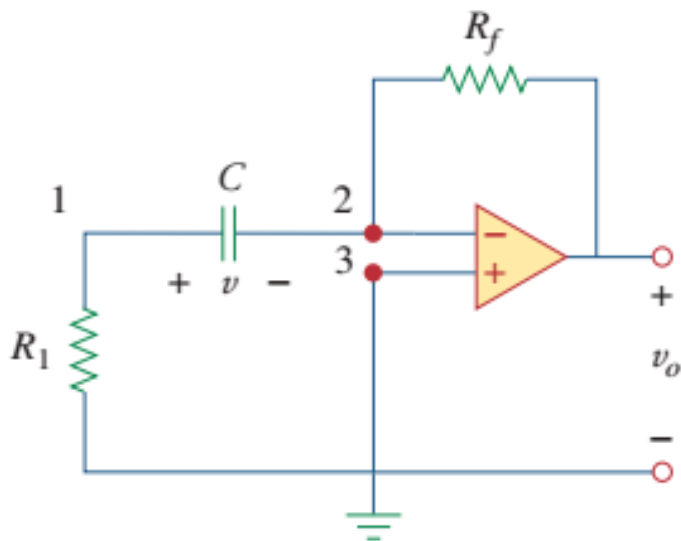For the op amp circuit in Fig. 7.55(a), find v_o for $t > 0$, given that $v(0) = 3 \text{ V}$. Let $R_f = 80 \text{ k}\Omega$, $R_1 = 20 \text{ k}\Omega$, and $C = 5 \mu\text{F}$.




(a)






Non-DC Sources

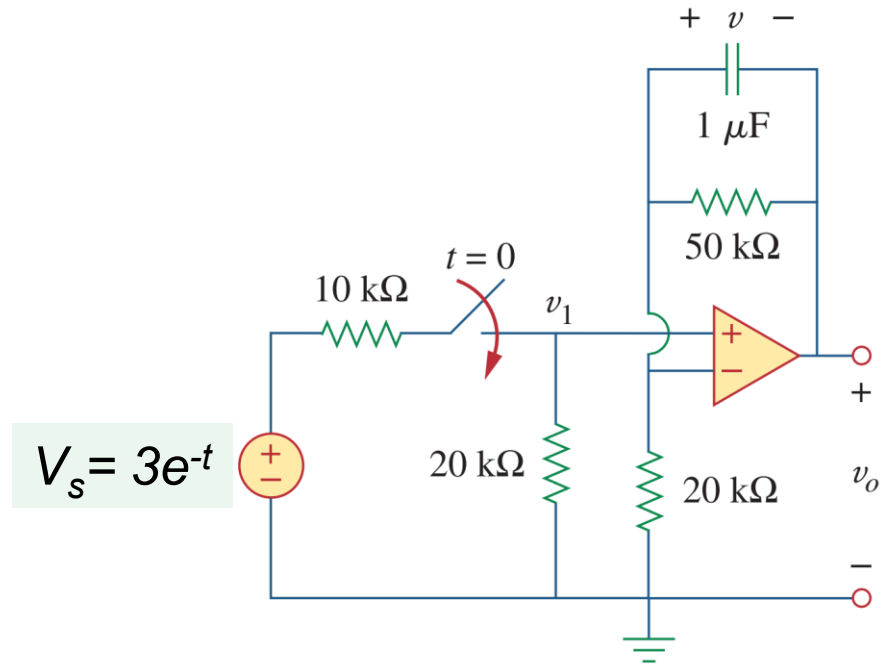





Practice

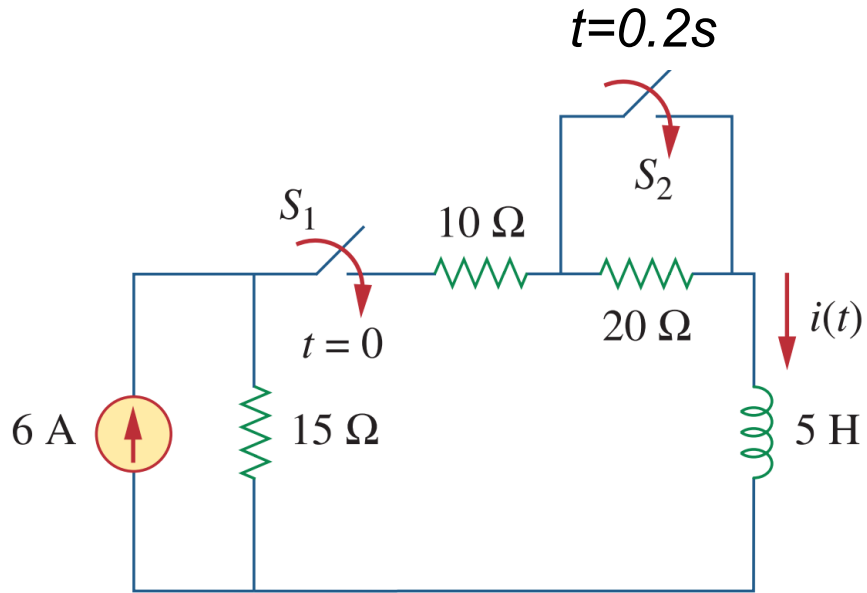



Practice

